

**PARUL UNIVERSITY**  
**FACULTY OF ENGINEERING & TECHNOLOGY**

**B.Tech. Summer 2018 - 19 Examination**

**Semester: 3****Subject Code: 03106203****Subject Name: Network Analysis****Date: 25/05/2019****Time: 2:00pm To 4:30pm****Total Marks: 60**

---

**Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

**Q.1 Objective Type Questions - (All are compulsory) (Each of one mark) (15)**

1. Write an equation of  $I_{TH}$ .
2. Draw the V-I characteristic for Ideal Voltage source
3. Super position theorem is applicable to \_\_\_\_\_ network.
4. The inductors act as an \_\_\_\_\_ circuit at time  $t = 0+$ .
5. Write an equation of  $I_L$  in Norton Theorem.
6. Transfer Function is \_\_\_\_\_ Transform of Output and Input Quantity.
7. Define: Poles and Zeros of network transfer function.
8. Define: Driving point impedance.
9. What is the condition for symmetrical network for z-parameters?
10. What is the condition for reciprocal network for h-parameters?
11. Define: Oriented Graph.
12. What is Tree and Co-tree?
13. Define: Tie-set.
14. Define: Incidence matrix.
15. Define: Cutset and Cutset Matrix.

**Q.2 Answer the following questions. (Attempt any three) (15)**

A) Find the current passing through the 2 Ohm resistor using Mesh analysis for the circuit shown in the following figure 1.

B) Explain Duality and draw a Dual Network of given Figure 2.

C) State Millman's theorem. Obtain the equivalent of a parallel connection of three branches each with a voltage source and a series resistance, (2V, 1 Ohm), (3V, 2 Ohm) and (5V, 2 Ohm).

D) Determine the node voltages V1 and V2 in the network shown in Figure-3 below by applying the superposition theorem.

**Q.3 A) Explain Relation Between Hybrid Parameter and ABCD Parameter. (07)**

B) Obtain Hybrid Parameter for given network (Figure-4). (08)

**OR**

B) Explain Relation Between g Parameter and Y Parameter (08)

**Q.4 A) Explain Transient R-L and Transient R-C Circuit. (07)**

**OR**

A) Explain Supermesh and Supernode in detail. (07)

B) Obtain Incidence Matrix, Loop Matrix and Cutset Matrix for given Figure-5.

(08)

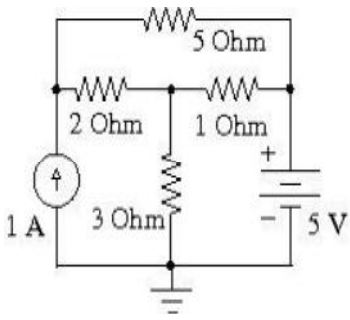


Figure-1

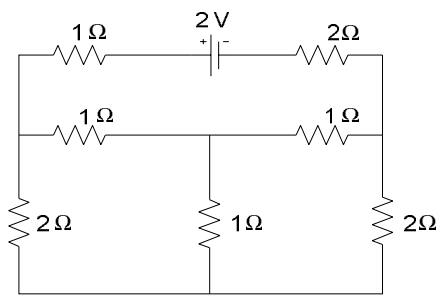


Figure-2

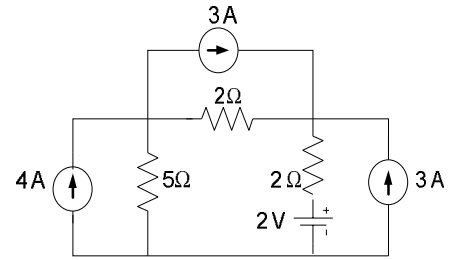


Figure-3

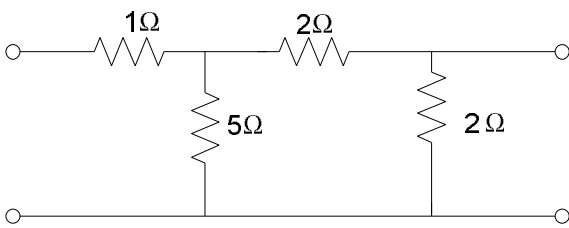


Figure-4

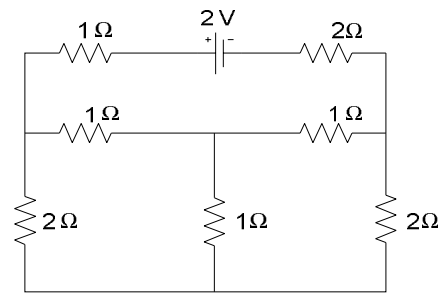


Figure-5