

**PARUL UNIVERSITY**  
**FACULTY OF ENGINEERING & TECHNOLOGY**

**B.Tech. Summer 2018 - 19 Examination**

**Semester: 3****Subject Code: 03107201****Subject Name: Advanced Analog Electronics****Date: 28/05/2019****Time: 02:00pm to 04:30pm****Total Marks: 60****Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

**Q.1 Objective Type Questions - ( Fill in the blanks, one word answer, MCQ-not more than Five in case (15) of MCQ) (All are compulsory) (Each of one mark)**

1. State various resistances and capacitances in the hybrid  $\pi$  model.
2. What is the maximum efficiency of a class B circuit?
  - a) 90 %
  - b) 78.5 %
  - c) 50 %
  - d) 25 %
3. Which type of power amplifier is biased for operation at less than  $360^\circ$  of the cycle?
4. The gate of JFET is \_\_\_\_\_ biased.
  - a) forward
  - b) reverse
  - c) forward
  - d) reverse as well as forward
  - e) none of above
5. A JFET has three terminals, namely.....
  - a) cathode, anode, grid
  - b) source, gate ,drain
  - c) emitter, base, collector
  - d) none of the above
6. Draw symbol of P Channel E - MOSFET
- 7.State type of feedback used in the oscillator circuits?
8. Write the formula of Gain with feedback for voltage shunt feedback connection
9. Draw the symbol of N Channel D - MOSFET
10. Define Pinch-off voltage with reference to JFET
11. What is the main difference between E-MOSFET and D-MOSFET?
12. Write the drain current equation for JFET.
- 13.A MOSFET is sometimes called ..... JFET
  - a) many gate
  - b) open gate
  - c) insulated gate
  - d) shorted gate
14. Which of the following oscillator is RC type:
  - a) Clapp
  - b) Hartley
  - c) Colpitt's
  - d) Phase Shift
15. The expression for frequency of oscillations of a RC phase shift oscillator is
  - a)  $f = 1 / (2\pi\sqrt{RC})$
  - b)  $f = 1 / (2\pi\sqrt{R(C1 + C2)})$
  - c)  $f = 1 / (2\pi RC\sqrt{6})$
  - d) none of the above

- Q.2 Answer the following questions. (Attempt any three) (15)**
- A) Obtain trans conductance value for  $I_c$  equal to 10 mA.
- B) (i) A class A transformer-coupled class A amplifier uses a 25:1 transformer to drive a 4 ohm load. Calculate the effective ac load. (ii) What transformer turns ratio required to match 16 ohm speaker load so that effective resistance seen at the primary is 10K ohm.
- C) Draw the AC equivalent circuit for JFET. What is the value of constant 'k' in E-MOSFET when  $V_{GS(ON)} = 8\text{ V}$ ,  $I_{D(ON)} = 10\text{ mA}$ ,  $V_{GS(TH)} = 2\text{ V}$ .
- D) Derive the formula for trans-conductance  $g_m$  in FET using mathematical approach and shockley's equation.
- Q.3 A) Draw the voltage series feedback connection. Also derive the input impedance & output impedance. (07)**
- B) State & Derive Barkhausen criterion required for oscillation (08)
- B) A transistor has following parameters at  $I_c = 10\text{mA}$ ,  $h_{ie} = 1\text{K}\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 100$ ,  $h_{oe} = 4 \times 10^{-5}\text{ A/V}$ . Calculate (i)  $g_m$  (ii)  $r_{b'e}$  (iii)  $r_{b'b'}$  (iv)  $r_{b'c}$  (08)
- Q.4 A) Explain the operation of class B Push Pull amplifier with circuit. (07)**
- A) Draw the VDB circuit for JFET. Also find  $Z_i$ ,  $Z_o$  and  $A_v$  (07)
- B) Determine the following parameters for the network given in the following figure. (08)
- $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DS}$ ,  $V_D$ ,  $V_G$ ,  $V_S$

