

**PARUL UNIVERSITY**  
**FACULTY OF ENGINEERING & TECHNOLOGY**  
**B.Tech. Summer 2018 – 19 Examination**

**Semester: 4**  
**Subject Code: 03112253**  
**Subject Name: Electronic Devices & Circuits**

**Date: 08/05/2019**  
**Time: 2:00 pm to 4:30pm**  
**Total Marks: 60**

---

**Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

---


**Q.1 Objective Type Questions (All are compulsory) (Each of one mark) (15)**

1. FET is \_\_\_\_\_ controlled device.
  - a) Current
  - b) Voltage
  - c) Power
  - d) Frequency
2. What is cascading?
3. What is the main advantage of Schottky diode?
4. Compute the value of  $\alpha$ , if  $\beta = 100$ .
5. Draw the symbol of NPN Transistor.
6. Draw graph of induced capacitance vs. reverse voltage in case of varactor diode.
7. What is the full name of MOSFET?
8. Knee voltage of Germanium diode is \_\_\_\_\_.
  - a) 0.7 V
  - b) 0.3 V
  - c) 0.6 V
  - d) 1 V
9. Size of collector is \_\_\_\_\_ compare to emitter.
10. What is the total current gain of darlington pair? (provided individual current gain of transistor 1 and transistor 2 are  $\beta_1, \beta_2$  respectively)
  - a)  $\beta_1 + \beta_2$
  - b)  $\beta_1 \beta_2$
  - c)  $\beta_1 / \beta_2$
  - d)  $\beta_1 - \beta_2$
11. Write any one application of transistor.
12. The input impedance of a transistor is \_\_\_\_\_.
  - a) high
  - b) low
  - c) very high
  - d) almost zero
13. Define 'Small signal amplifier'.
14. Why negative feedback concept is used for amplifier?
15. Define 'Collector Efficiency' with respect to power amplifier.

---

**Q.2 Answer the following questions. (Attempt any three) (15)**

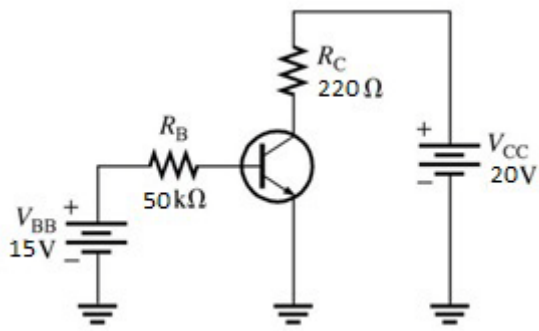- A) What do you mean by Opto-electronic devices? Explain any one in detail with necessary diagram.
- B) Explain voltage shunt feedback topology of an amplifier with diagram.
- C) Draw the load line and locate operating point for the given circuit. Assume  $\beta_{dc}=100$ .



D) Differentiate between BJT and FET.

- Q.3** A) Explain working of Zener as voltage regulator. (07)  
 B) List different type of power amplifiers. Explain working of class B push-pull amplifier. (08)

**OR**

- B) Explain the concept of multistage amplifier. List types of coupling and explain any one type of coupling. (08)

- Q.4** A) List the types of transistor biasing. Illustrate any one biasing method in detail. Use diagram and equations, wherever required. (07)

**OR**

- A) Draw and explain overall working of CE amplifier circuit and working of all the components available in the circuit. Also draw the necessary waveform. (07)  
 B) (i) Derive the relation between  $\alpha$  and  $\beta$  of BJT. (08)  
 (ii) Calculate  $I_B$ ,  $\beta$ ,  $\alpha$ ,  $I_{CBO}$ . Provided that  $I_E=10\text{mA}$ ,  $I_C=9.91\text{mA}$ .