

PARUL UNIVERSITY
FACULTY OF ENGINEERING & TECHNOLOGY
B.Tech. Summer 2018-19 Examination

Semester: 5**Subject Code: 03106304****Subject Name: Industrial Electronics II****Date: 22/05/2019****Time: 10:30am to 1:00pm****Total Marks: 60****Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

Q.1 Objective Type Questions**(15)**

1. Harmonics in 3 phase inverters can be reduced by
 - a) active filters
 - b) passive filters
 - c) none of these
 - d) all of the mentioned
2. In current source inverters (CSIs)
 - a) the amplitude of the output current is independent of the load
 - b) the amplitude of the output current depends on the load
 - c) the amplitude of the output voltage is independent of the load
 - d) none of the mentioned
3. In the principle of phase control
 - a) the load is on for some cycles and off for some cycles
 - b) control is achieved by adjusting the firing angle of the devices
 - c) control is achieved by adjusting the number of on off cycles
 - d) control cannot be achieved
4. In a full bridge VSI, in order to avoid the short circuit across the DC bus and the undefined AC output voltage condition, the modulating technique should ensure that
 - a) Top switch of each leg is on at any instant
 - b) Bottom switch of each leg is on at any instant
 - c) Either (a) or (b)
 - d) None of these
5. In square wave operation mode of 3 phase VSI, the VSI
 - a) Can control the load voltage
 - b) Cannot control the load voltage
 - c) Cannot control the load voltage except by means of dc link voltage
 - d) Cannot control the load voltage except by means of dc link current
6. In the 180° mode VSI, _____ devices conduct at a time.
7. The 120° mode of operation of a three phase bridge inverter requires _____ number of steps.
8. In the PWM method, _____ order harmonics are minimized.
9. In SPWM the modulating signal is _____.
10. In voltage fed thyristor inverters _____ commutation is required.
11. If energy is taken from the AC side of the inverter and sends it back into the DC side, then it is known as _____.

12. In a 3 phase bridge rectifier the ripple frequency is _____ times input frequency.
13. The shape of the output voltage waveform in a single PWM is _____.
14. In sinusoidal pulse width modulation, _____ wave is compared with a _____ type of wave.
15. _____ and _____ can also be called as commutating components.

Q.2 Answer the following questions. (Attempt any three) (15)

- A) Compare on-off control and phase angle control
- B) What are the advantages and disadvantages of cycloconverter?
- C) Discuss about Static Relay.
- D) Compare different PWM Techniques

Q.3 A) What is cycloconverter? Explain its basic working by single phase to single phase cycloconverter. (07)

B) Draw and explain single phase ac to ac voltage controller with RL Load. (08)

OR

B) Discuss single phase current source inverter. Give comparison between CSI and VSI (08)

Q.4 A) With waveforms and figure write a note on 3 phase load commutated CSI. (07)

OR

A) Explain three phase inverter working of 120 degree mode of conduction with power circuit, conduction sequences and waveforms. (07)

B) Write a Short Note on Parallel Inverter with waveforms. (08)