

**PARUL UNIVERSITY**  
**FACULTY OF ENGINEERING & TECHNOLOGY**  
**B.TECH MID SEM EXAMINATION**  
**3<sup>RD</sup> SEMESTER**  
**ACY-2022-23 (ODD SEM)**

Subject Name: Electrical Circuit Analysis (203106205)

Branch: Electrical Engineering

Date: 05/08/2022

Time: 02:30 PM-04:00 PM

Total Marks: 40


Sr. No.

Marks


Q.1 (A)

05

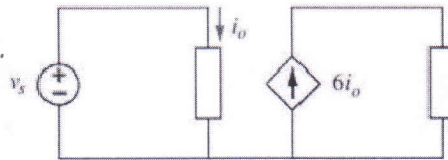
1. Find current flowing in a dielectric material due to a charge of 60 C after 12 s.
2. The dependent source in fig. is \_\_\_\_\_.



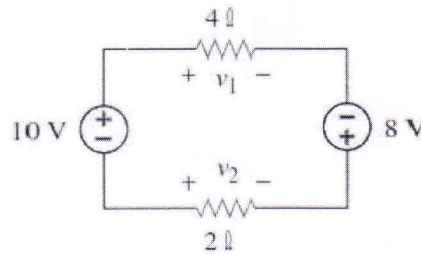3. Find  $V_2$  in the circuit of figure.




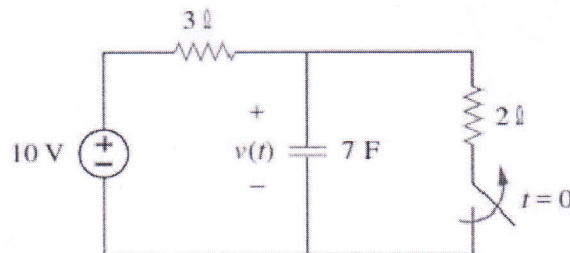4. In the circuit of figure, find the voltage drop across  $2 \Omega$  just before  $t = 0$ .



5. Obtain time constant for an series R-C circuit with  $R = 2 \Omega$  and  $C = 10 \mu\text{F}$ .
- (B) Calculate power delivered by 3 A in the below circuit using nodal analysis.


05

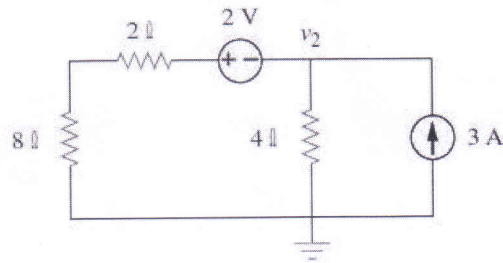


Q.2 Attempt any four(Short Questions)

12

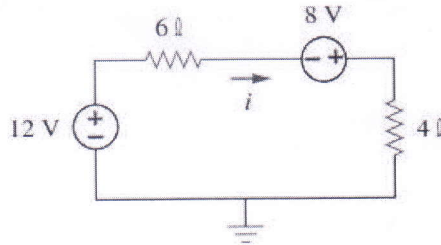
(1) Evaluate voltage drop across  $6 \Omega$  resistor in the below circuit.



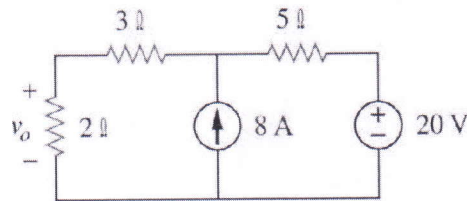
(2) Using the superposition theorem, find  $V_0$  in the circuit in figure.



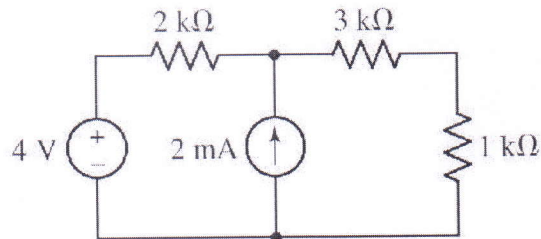
(3) Find thevenin's equivalent circuits for given network faced by the  $3 \text{ k}\Omega$  resistor.



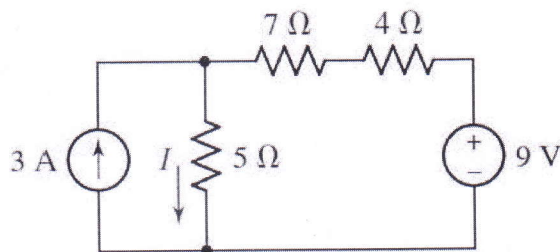(4) Determine the current 'I' in the circuit of figure by performing source transformations



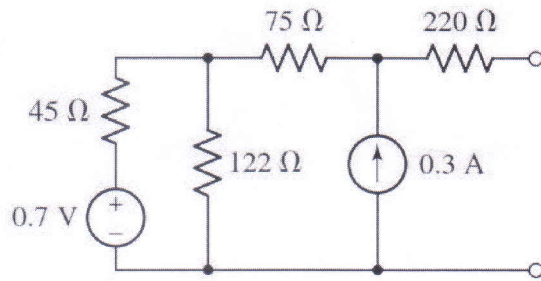
(5) Employ Norton's theorem to obtain a simple two-component equivalent of the circuit shown in figure.




Q.3 Attempt any two

08

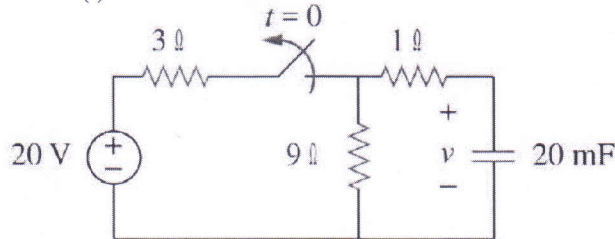
- (1) The switch in the circuit in figure has been closed for a long time, and it is opened at  $t = 0$ . Find  $v(t)$  for  $t > 0$ .



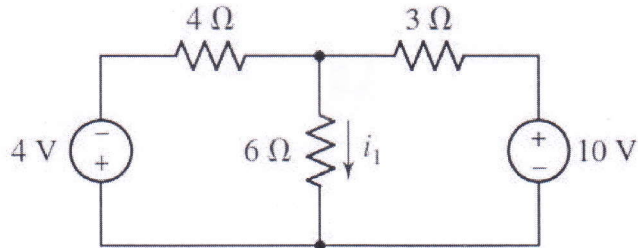- (2) Verify Tellegen's theorem in below circuit.




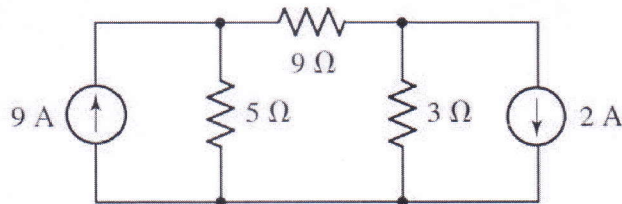- (3) With reference to the circuit of figure calculates the power absorbed by the 9 Ω resistor.



- Q.4 (A) The switch in figure has been closed for a long time. It opens at  $t = 0$ . Find  $i(t)$  for  $t > 0$ .


05

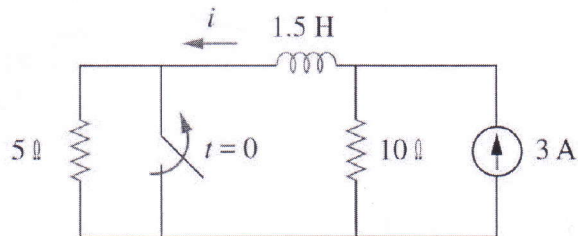

- (B) Derive the condition for maximum power transfer from source to load in given

05

circuit

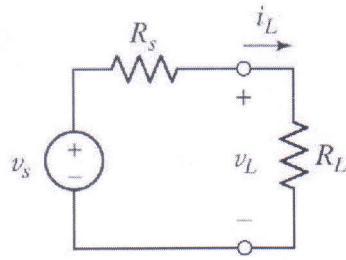

OR

(B) For the circuit in figure, find

- (a)  $i(0^+)$  and  $v(0^+)$
- (b)  $i(\infty)$  and  $v(\infty)$
- (c)  $\frac{di(0^+)}{dt}$  and  $\frac{dv(0^+)}{dt}$

05

