

**PARUL UNIVERSITY**  
**FACULTY OF ENGINEERING & TECHNOLOGY**  
**B.Tech. Winter 2019 - 20 Examination**

**Semester: 5****Subject Code: 03106304****Subject Name: Industrial Electronics- II****Date: 05/12/2019****Time: 10:30am to 01:00pm****Total Marks: 60****Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

**Q.1 Objective Type Questions - ( Fill in the blanks, one word answer, MCQ-not more than Five in case (15) of MCQ) (All are compulsory) (Each of one mark)**

1. Several equidistant pulses per half cycle are used in \_\_\_\_\_ type of modulation technique.
  - a) single-pulse
  - b) multiple-pulse
  - c) sine-pulse
  - d) equidistant-pulse
2. The modulation index (MI) is given by  
 $V_r$  = peak value of the reference wave.  
 $V_c$  = peak value of the carrier wave.
  - a)  $V_r/V_c$
  - b)  $V_c/V_r$
  - c)  $(1 + V_c/V_r)$
  - d)  $1/(V_c V_r)$
3. In a PWM inverter, if the frequency of the lowest harmonic is 180 Hz, then the frequency of the fundamental component would be \_\_\_\_\_.
  - a) 50 Hz
  - b) 60 Hz
  - c) 540 Hz
  - d) 90 Hz
4. In an inverter, if the fundamental output frequency is 45 Hz, then the frequency of the lowest order harmonic will be
  - a) 45 Hz
  - b) 225 Hz
  - c) 15 Hz
  - d) 135 Hz
5. Which of the following is used as a harmonic reduction technique in inverters?
  - a) Amplitude modulation
  - b) Cycloconverter control
  - c) Transformer connection
  - d) Series connection of two inverters
6. In sinusoidal pulse width modulation, \_\_\_\_\_ wave is compared with a \_\_\_\_\_ type of wave.
7. The waveform obtained by \_\_\_\_\_ Circuit is more near to a sinusoidal wave.
8. A single-phase half wave voltage controller consists of one SCR is anti parallel with one \_\_\_\_\_.
9. In a single-phase half wave inverter \_\_\_\_\_ SCR(s) are/is gated at a time.
10. In the  $180^\circ$  mode VSI, \_\_\_\_\_ devices conduct at a time.
11. In single-phase modulation of PWM inverters, the lowest harmonic can be eliminated if the pulse width is made equal to \_\_\_\_\_.
12. In pulse width modulated inverters, the output voltage is controlled by controlling the \_\_\_\_\_.
13. \_\_\_\_\_ is used for critical loads where temporary power failure can cause a great deal of inconvenience.
14. Voltage Controllers convert the fixed ac voltage to variable ac by changing the values of \_\_\_\_\_.
15. The single phase bridge type cycloconverter uses \_\_\_\_\_ number of SCRs.

- Q.2 Answer the following questions. (Attempt any three)** (15)
- A) Explain why a PWM inverter is superior to square wave inverters?
  - B) Compare on off control and phase angle control.
  - C) Compare on VSI and CSI.
  - D) A Short Note on UPS with block diagram.
- Q.3** A) Derive the expression for the RMS value of output voltage for the 1 phase half wave controller circuit. (07)
- B) A single phase half bridge inverter has a resistive load of  $R = 10$  ohms. DC input voltage  $V=48V$ . Determine : (08)
- 1. The rms output voltage at the fundamental frequency,  $V_1$
  - 2. The output power,  $P_o$
  - 3. The average and peak currents of each transistor.
- OR**
- B) A single phase bridge inverter has a resistive load of  $R=24$  ohms and dc input voltage  $V=48V$ . (08)
- Determine :
- 1. The output power,  $P_o$
  - 2. The average and peak currents of each transistor.
  - 3. The peak reverse blocking voltage  $V_{BR}$  for each transistor.
- Q.4** A) What is PWM ? Explain SPWM Techniques. (07)
- OR**
- A) Write a short note on Solid State Relays. (07)
- B) What is the principle of operation of Cycloconverters ? Explain Single phase to Single phase Circuit of Cycloconverter. (08)