

PARUL UNIVERSITY
FACULTY OF ENGINEERING & TECHNOLOGY
B.Tech. Winter 2022-23 Examination

Semester: 3

Subject Code: 203107201

Subject Name: Electronic Devices

Date: 06/10/2022

Times: 2.00 pm to 4.30 pm

Total Marks: 60

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

Q.1 Objective Type Questions - (Fill in the blanks, one word answer, MCQ-not more than Five in case of MCQ) (All are compulsory) (Each of one mark) **(15)**

1. MOSFET stands for _____.
2. Barrier potential of silicon _____ and germanium _____.
3. The alternative name of Chip IC is Wafer. True/False
4. Components which are not producing gain are called _____.
5. FET stands for _____.
6. When negative voltage feedback is applied to an amplifier, its voltage gain _____.
 - a) Is increased
 - b) Is reduced
 - c) Remains the same
 - d) None of the above
7. In an LC transistor oscillator, the active device is _____.
 - a) LC tank circuit
 - b) Biasing circuit
 - c) Transistor
 - d) None of the above
8. An oscillator converts _____.
9. Full form of LED _____.
10. MOSFET works on _____ principle.
11. Which among the below mentioned devices acts as a driver in CMOS Inverter Circuit?
 - a) PMOS
 - b) NMOS
 - c) Both a and b
 - d) None of the above
12. Formula for voltage gain _____.
13. Full form of CMOS _____.
14. Photodiode works in _____ biasing.
15. In CMOS process oxidation process is carried out using _____.

Q.2 Answer the following questions. (Attempt any three) **(15)**

- A) Explain difference between conductor, semiconductor and insulator along with its Energy band diagram.
- B) Explain Difference between 1)MOSFET and CMOS
2)PMOS and NMOS
- C) Explain the following terms.
 - i) Diffusion current
 - ii) Drift current
 - iii) Mobility
 - iv) Resistivity
 - v) Stability
- D) Explain steps for Twin tub CMOS fabrication process.

Q.3 A) Explain multistage amplifiers with its input and output wave form along with its frequency responses. **(07)**

- B) What do you mean by Oscillator? Explain the Barkhausen Criterion along with advantages of oscillator circuit. **(08)**

OR

- B) What do you mean by Amplifier? Explain different class of it and explain any one of them. **(08)**

Q.4 A) What do you mean by feedback topologies? Explain different types of it. **(07)**

OR

- A) Explain Hartley oscillator and a Colpitts oscillator with its advantages. **(07)**

- B) Explain in detail about LED, photodiode and solar cell with its pros and cons. **(08)**