

PARUL UNIVERSITY
FACULTY OF ENGINEERING & TECHNOLOGY
B.Tech. Summer 2022 - 23 Examination

Semester: 4th
Subject Code: 203112259
Subject Name: Electronic Devices & Circuits

Date: 27-3-2023
Time: 2.00 pm to 4.30 pm
Total Marks: 60

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

Q.1 Objective Type Questions -**(15)**

1. The primary function of the bias circuit is to
 - a) hold the circuit stable at VCC
 - b) hold the circuit stable at v_{in}
 - c) ensure proper gain is achieved
 - d) hold the circuit stable at the designed Q-point
2. The capacitor that produces an ac ground is called a(n)
 - a) coupling capacitor
 - b) dc open
 - c) bypass capacitor
 - d) ac open
3. In a class B push-pull amplifier, the transistors are biased slightly above cutoff to avoid
 - a) crossover distortion
 - b) unusually high efficiency
 - c) negative feedback
 - d) a low input impedance
4. The value of V_{BE} in active region in NPN transistor
 - a) 0.7V
 - b) 1V
 - c) 0V
 - d) 5V
5. Which of the following is not an electronic device?
 - a) Mobile
 - b) Computer
 - c) Magnifying glass
 - d) Keyboard
6. The voltage gain (A_v) of any transistor amplifier circuit equals the _____.
7. The gain of a BJT is called _____.
8. Reverse bias is a condition that essentially _____ current through the diode.
9. Atoms that normally have three electrons in their outer shell are called _____ atoms.
10. Size of collector is _____ compare to emitter.
11. Draw the symbol of NPN transistor.

12. Draw the symbol of PNP transistor.

13. What is the current gain for a common-base configuration where $I_E = 4.2 \text{ mA}$ and $I_C = 4.0 \text{ mA}$?

14. If a 3 mV signal produces a 2 V output, what is the voltage gain?

15. What is the collector current for a C-E configuration with a beta of 100 and a base current of $30 \mu\text{A}$?

Q.2 Answer the following questions. (Attempt any three) **(15)**


1. Compare LED and photodiode.
2. Explain varactor diode with necessary circuit diagram.
3. Explain schottky diode with necessary circuit diagram.
4. If the base current of transistor is $20 \mu\text{A}$ when the emitter current is 5.2 mA, what are the values of β and α ?

Q.3 A) Explain & draw voltage divider biasing & derive its voltage gain using AC analysis. **(07)**

B) Explain operation of class -B amplifier with the help of circuit and wave form. **(08)**

OR

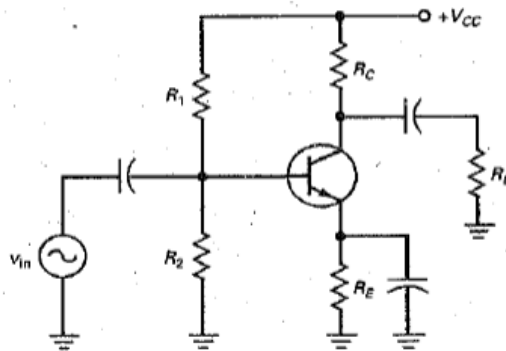B) Draw ac equivalent circuit of given figure. **(08)**



Q.4 A) Explain and draw the circuit of n-channel JFET also derive its drain current. **(07)**

OR

A) Explain the fixed bias network for BJT & derive its DC voltage & current. **(07)**

B) Explain & draw voltage divider biasing & derive its DC voltage & current. **(08)**