

PARUL UNIVERSITY
FACULTY OF ENGINEERING & TECHNOLOGY
M.Tech. Winter 2018 -19 Examination

Semester: 1**Subject Code: 203212102****Subject Name: CMOS CIRCUIT DESIGN - I****Date: 11/12/2018****Time: 10:30am to 1:00pm****Total Marks: 60****Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

Q.1 A) Define: Regularity, Modularity, Locality (05)

B) Why analog circuit fundamental necessary in recent era ? (05)

C) Explain the simplified view of VLSI design flow in detail. (05)

Q.2 Answer the following questions. (Attempt any three) (Each five mark) (15)

A) Explain the basics of current mirrors with necessary circuit diagrams.

B) Discuss Fabrication process steps for nMOS transistor.

C) Explain the gradual channel approximation for the MOSFET V-I characteristics.

D) Explain the miller's theorem in detail.

Q.3 A) Explain in detail: Gilbert cell (07)

B) Explain in brief: single ended and differential operations. (08)

OR

B) Explain the qualitative analysis in detail for the basic differential pair. (08)

Q.4 A) Explain small signal and large signal circuit for common source single stage amplifier with resistive load. (07)

OR

A) Define Amplifier and explain the characteristics of amplifier and why it is important. (07)

B) Explain the MOSFET scaling. (08)