

PARUL UNIVERSITY
FACULTY OF ENGINEERING & TECHNOLOGY
M.Tech., Summer 2017 - 18 Examination

Semester: 2
Subject Code: 03204183
Subject Name: RF Circuit Design

Date: 28/05/2018
Time: 02:00 pm to 04:30 pm
Total Marks: 60

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

Q.1 A) Explain the following terms: **(05)**

1) Decibel 2) Bandwidth 3) Insertion Loss 4) Shape Factor 5) Ripples

B) Explain why skin effect are considered important for RF circuit design. **(05)**

C) Proof that P_{out} maximum occurs when $R_L=R_S$. **(05)**

Q.2 Answer the following questions. (Attempt any three) (Each five mark) **(15)**

A) What are the two basic approaches in handling of matching of complex impedance ?

B) Discuss about T matching network.

C) What is dual network? Explain its step with an example and also mention the advantages of dual network.

D) A transistor has the following Y parameters at 100 MHz, with $V_{CE}=10$ volts and $I_C =5$ mA. $Y_i= 8 + j5.7$ mmho, $Y_o= 0.4 + j1.5$ mmho, $Y_{r}= 52 - j20$ mmho, $Y_{f}= 0.01 - j0.1$ mmho
 Calculate Criteria C and MAG.

Q.3 A) Explain Bipolar and Field Effect Transistor. Compare with an appropriate point of view. **(07)**

B) What is barkhausen criteria of oscillation? Explain it with basic oscillator model. **(08)**


OR

B) Describe briefly how passive components are realized on printed circuit board at RF. **(08)**

Q.4 A) What is band pass filter and band reject filter. Define its transformation procedure from the low pass filter. **(07)**

OR

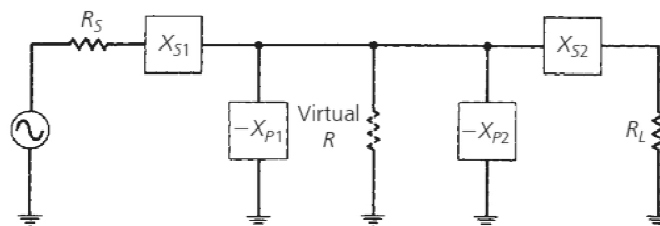A) Using Fig. as a reference for T- Network, design four different networks to match a 10-ohm source to a 50-ohm load. Each network is to have a loaded Q of 10. **(07)**



B) What is smith chart? Write down its application and characteristics. **(08)**