

PARUL UNIVERSITY
FACULTY OF ENGINEERING & TECHNOLOGY
M.Tech., Summer 2017 – 18 Examination



Semester: 2
Subject Code: 03212152
Subject Name: Cmos Circuit Design-II

Date: 21/05/2018
Time: 2:00 pm to 4:30 pm
Total Marks: 60

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Start new question on new page.

  - Q.1** A) With neat sketch explain the basic architecture of DRAM. (05)
 B) Draw the basic circuit of a switched capacitor, its equivalent circuit, explain its operation and derive its equivalent resistor value. (05)
 C) Describe basic PLL topology. (05)
- Q.2** Answer the following questions. (Attempt any three) (Each five mark) (15)
- A) Explain detail procedure for input matching using LNAS.
 B) What is a flash converter? Discuss the working of a 3-bit flash A/D Converter.
 C) Explain delay locked loops in PLLs.
 D) Design unit gain sampler circuit using Op-amp.
- Q.3** A) Design start up circuit for band gap reference. (07)
 B) Calculate V_{out} for the given circuit. Assume $\lambda = 0$. (08)



OR

- B) A type- I PLL experiences a frequency step $\Delta\omega = 0$ at $t = 0$. Calculate the change in phase error. (08)
- Q.4** A) Explain PTAT current generator circuit. (07)
- OR**
- A) Design pre amplification stage of comparator using NMOS and PMOS. (07)
 B) Give detail about MOSFET as a complementary switch with circuit diagram. (08)